

Circuits Tool Box (Conclusions for Series and Parallel Circuit Lab)

Type of Circuit	Path of Electron	Voltage	Current	Equivalent Resistance	Type of Circuit
		V	I	R_{eq}	
Series	No Choice	Adds	Same	$R_{eq} = R_1 + R_2 + R_3$	Series
Parallel	Choice	Same for each branch	Adds for each branch	$1/R_{eq} = 1/R_1 + 1/R_2 + 1/R_3$	Parallel

Best way to do **Parallel R_{eq}** is take the resistors **2 at a time** and do **POS (Product over Sum)**

$$R_1 R_2 / (R_1 + R_2)$$

$V = IR$ Voltage = Current * Resistance (Ohm's Law) **R is slope of Voltage-Current graph**

$P = IV$ Power = Current * Voltage (also **$P = I^2 * R$**) **P is area of rectangle of Voltage-Current graph**

Current = Brightness = Power (for a set voltage) Powers of Resistances **ALWAYS ADDS** to = Power of Voltage Source

Resistance in wire is assumed zero. However in reality, the longer the wire is the more resistance it has. Also, the hotter a wire is the more resistance it has.

Also: **Ammeters** measure Current going THROUGH wires and circuit elements are **ALWAYS** hooked in SERIES and always have extremely LOW RESISTANCE. You have to BREAK a circuit and INSERT an Ammeter. Symbol is:

Voltmeters measure Voltage ACROSS wires and circuit elements and are **ALWAYS** hooked in Parallel and always have extremely HIGH RESISTANCE. You NEVER BREAK a circuit and INSERT an Ammeter. Symbol is: